





PART - B

(5×16=80 Marks)

11. a) i) Analyse the given circuit Fig. 11 (a) and obtain the voltage across all elements, impedance, current, power factor and hence draw the phasor diagram. (13)

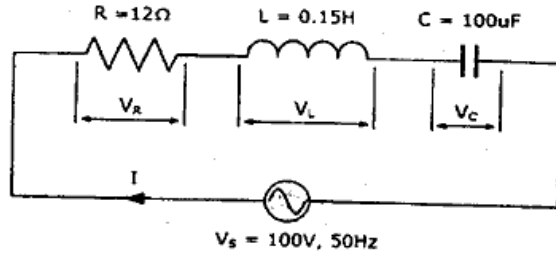


Fig. 11 (a)

- ii) Explain the significance of power factor circuit. (3)  
(OR)

- b) Use nodal analysis to find the voltage at each node of this circuit. Shown in Fig. 11 (b). (16)

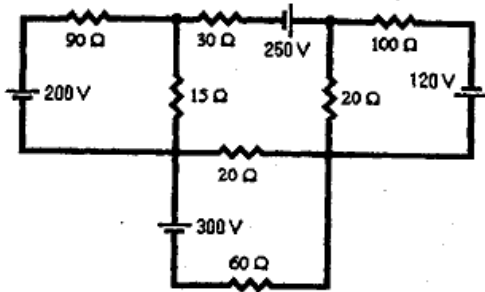


Fig. 11 (b)

12. a) Find the maximum power transferred to the load using maximum power transfer theorem for the circuit shown in Fig. 12 (a). (16)

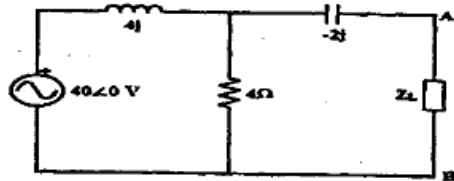


Fig. 12 (a)

(OR)



- b) Find the equivalent resistance across terminal AB in the circuit shown in Fig. 12 (b) and find the current supplied by the source. (16)

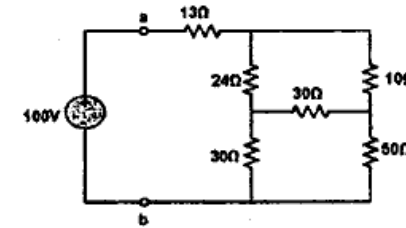


Fig. 12 (b)

13. a) A series L-R-C circuit has a sinusoidal input voltage of maximum value 12 V. If inductance,  $L = 20 \text{ mH}$ , resistance,  $R = 80 \Omega$  and capacitance,  $C = 400 \text{ nF}$ , determine (a) the resonant frequency, (b) the value of the p.d. across the capacitor at the resonant frequency, (c) the frequency at which the p.d. across the capacitor is a maximum and (d) the value of the maximum voltage across the capacitor. (16)

(OR)

- b) Find the vector values of the currents in the network shown in Fig. 13 (b). Find also the power supplied by each source. (8+8)

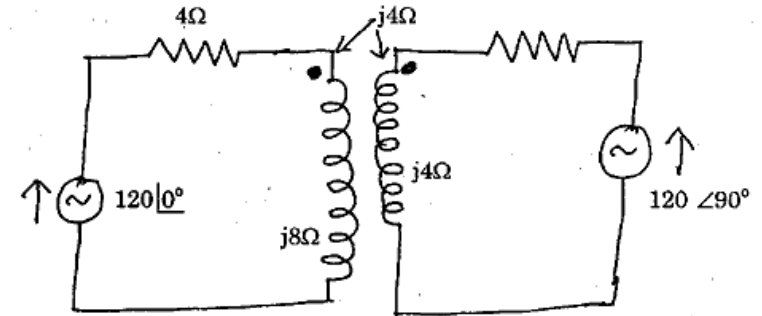


Fig. 13 (b)

14. a) A series RL circuit with  $R = 100 \text{ ohms}$  and  $L = 20 \text{ H}$  has a DC voltage of 200 volts applied through a switch at  $t = 0$ . Find :  
a) The equation for the current and voltages across the different elements  
b) The current at  $t = 0.5$  seconds  
c) The current at 1 second and  
d) The time at which  $e_R = e_L$ . (3+3+3+7)

(OR)