



V Semester B.Sc. Examination, October/November 2012
(Semester Scheme)

PHYSICS – V

Gravitation, Space Physics and Electronics

Time : 3 Hours

Max. Marks : 60

Instruction : Answer any five questions in Part A, any four in Part B and five in Part C.

PART – A

Answer any five of the following :

(5×6=30)

1. a) Define gravitational potential at a point.
b) Obtain an expression for the gravitational potential due to a uniform solid sphere at a point outside the sphere. (1+5)
2. a) What is escape velocity ? Explain.
b) Derive an expression for the escape velocity of a body on the earth. (2+4)
3. a) What is relative humidity ?
b) Outline the vertical structure of the atmosphere. (1+5)
4. a) What are hybrid parameters of a transistor ?
b) Draw an AC equivalent circuit of a CE transistor amplifier and derive expressions for voltage gain and current gain using h-parameters. (1+5)
5. a) Define any two JFET parameters.
b) With the help of a circuit diagram describe the action of a zener diode as a voltage regulator. (2+4)
6. a) What is an operational amplifier ? Why is it called so ?
b) Explain with circuit diagram, how an op-Amp can be used as an integrator. Obtain expression for its output voltage. (2+4)

P.T.O.



7. a) What are the essential parts of an oscillator ?
 b) Explain with circuit diagram, the working of a Hartley oscillator. Write the expression for its frequency. (2+4)
8. a) What is NOR gate ? Write the truth table for NOR.
 b) With the help of a circuit diagram and truth table, explain the working of a half adder circuit using logic gates. (2+4)

PART - B

Solve any four problems :

(4×5=20)

9. A satellite is circling round the earth at a height of 1000 Km above the earth's surface. Calculate the orbital velocity and period of revolution. Given, Radius of the earth = 6,400 Km; $g = 9.8 \text{ ms}^{-2}$.
10. In a transistor the base current and the collector current are $100 \mu\text{A}$ and 2mA respectively. Calculate I_E , α and β of the transistor.
11. In a Colpitt's oscillator, the inductance and capacitances in the tuned circuit are 16 mH , $0.016 \mu\text{F}$ and $0.018 \mu\text{F}$. Calculate the frequency of the oscillator.
12. a) Convert $[675]_8$ to binary.
 b) Convert $[AF.2F]_{16}$ to decimal and binary equivalents. (2+3)
13. Prove that

$$(A + B)(\overline{A} \overline{C} + C)(\overline{B} + \overline{A} C) = \overline{A} B$$
 Draw the logic circuit for the output.
- 14) Find the output of a three input summing op-Amp given the following data
 $V_1 = 2\text{V}$, $V_2 = 3\text{V}$, $V_3 = -1\text{V}$
 $R_1 = 15 \text{ K}\Omega$, $R_2 = 60 \text{ K}\Omega$, $R_3 = 600 \text{ K}\Omega$, $R_f = 60 \text{ K}\Omega$.
 Draw the diagram.

PART - C

(5×2=10)

Answer **any five** of the following :

15. a) Saturn is about sixtimes farther from the sun than the Mars. Which of the two planets has (a) longer period of revolution (b) larger orbital speed ?
- b) A junction transistor is called a bipolar transistor. Why ?
- c) Explain the concept of virtual ground in op-amp circuit.
- d) An oscillator is an amplifier with infinite gain. Justify.
- e) Does electric field exist across the depletion layer of a semiconductor diode ? Explain.
- f) A NAND gate is called a universal gate. Justify.
- g) Do gravity waves appear only in water ? Explain.
- h) A zener diode is a constant voltage source. Explain.
-